EC ENGR 3 Lab 1B Week 1 Lab 1

Multi-Meter Measurements

| 1. | Resistor # | Marked | DMM Measured | % Deviation from Marked |
|----|------------|--------|--------------|-------------------------|
| | R1 | 3.3ΚΩ | 3.238ΚΩ | 1.9% |
| | R2 | 2.2ΚΩ | 2.159ΚΩ | 1.8% |
| | R3 | 1ΚΩ | 1.004ΚΩ | 0.4% |

The % Deviation is less than the indicated tolerance.

- 2. 1200 ohms is within 20% of 1000 ohms, thus 1200 ohms at 20% would overlap with 1500 ohms and 1000 ohms.
- 3. a.

R1 Color Code Value: 2.2K R1 Measured Value: 2.176K R2 Color Code Value: 100K R2 Measured Value: 99.5K

b.

RSeries Value: 101.6K RParallel Value: 2.148K

C.

RSeries Resistance Calculated: 101.7 Measured: 101.6 % Difference: 0.1% RParallel Resistance Calculated: 2.129 Measured: 2.148 % Difference: 0.9%

- d. In the parallel connection, the smaller resistor dominates.
- e. In the series connection, the larger resistor dominates.

Measuring Internal Resistance of a Power Supply

Unloaded voltage (i.e. without 5 Ω resistor): 6.15 V

Loaded voltage (with 5 Ω resistor): 6.144 V

Voltage shift: 0.006 V

Calculate internal resistance: (Hint: The voltage divider equation will be useful here):

Vx = V0 R1/(R1+R2)

Vx = 6.144

V0 = 6.15

R1 = 5

Solving for R2 gets the resistance of 0.00488 ohms

<u>Unloaded and Loaded Voltage Dividers</u>

| 5. | | Unloaded Voltage Divider | Loaded Voltage Divider |
|----|------------------------|--------------------------|------------------------|
| | Vout (measurement) | 3.131 V | 2.695V |
| | Vupper1K (calculation) | 2.869 V | 3.305V |
| | Itotal (calculation) | 0.003131 amps | 0.003305 amps |

The increase in total current lowers the output voltage of the loaded voltage divider circuit because it goes through more resistance and there is more of a voltage drop in the first resistor.

Validation of Kirchhoff's Laws

| 2. | Measurement | Value |
|----|-------------|--------|
| | Α | 5.040 |
| | В | -1.674 |
| | С | -1.691 |
| | D | -1.676 |
| | Е | 0 |
| | F | 1.689 |
| | G | 0 |

- 3. Add measurements A through D: -0.001
- 4. Add measurements C, E, F, and G: -0.002

| 6. | Measurement | Value |
|----|-------------|--------|
| | Α | 5.038 |
| | В | -1.786 |
| | С | -1.465 |
| | D | -1.788 |
| | E | 0.732 |
| | F | 0 |
| | G | 0.729 |

| 7. | Resistor | Current | Choose One |
|----|----------|----------|------------|
| | В | 0.001786 | Entering |
| | С | 0.001465 | Leaving |
| | G | 0.000331 | Leaving |

| 9. 0.0001. Yes, because the measurements summed to 0 and the current through the node was conserved. |
|--|
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |
| |